

JK den D' 'ye $\rightarrow$


J	K	Q
0	1	0
1	0	1

$$J = D$$

$$K = J'$$

<u>Öncel</u>	<u>Sonrak</u>
0000	0001
0001	0011
0010	0101
0011	0010
0100	1000
0101	0010
0110	0010
0111	0010
1000	1101
1001	0010
1010	0010
1011	0010
1100	0010
1101	0000
1110	0010
1111	0010

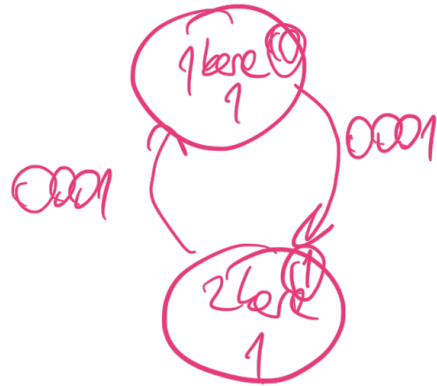$\rightarrow$ g kaç kere 1 geldiyse göre 1-1 mi 1-2 mi geçti olduğunu belirlem.



<u>Öncel</u>	<u>giriş</u>	<u>Sonrak</u>	<u>J_g</u>	<u>K_g</u>
0	0001	1	1	1
1	0001	0	1	1
0000			0	0

$$J_g = Q_3', Q_2', Q_1', Q_0 = K_g$$

$$g = Q_g$$

$Q_3 Q_2 Q_1 Q_0$	01	11	10
000	0	0	0
001	0	1	0
010	0	0	0
011	1	0	0

$$J_3 = Q_3 \cdot Q_2' \cdot Q_1' \cdot Q_0' + Q_3' \cdot Q_2 \cdot Q_1' \cdot Q_0$$

$$K_3 = J_3'$$

$Q_3 Q_2 Q_1 Q_0$	01	11	10	
000	0	g	0	1
001	1	0	1	1
010	1	0	1	1
011	0	1	1	1

$$J_1 = g \cdot Q_3' \cdot Q_2' \cdot Q_1' \cdot Q_0 + Q_2 \cdot Q_0'$$

$$+ Q_3 \cdot Q_2' \cdot Q_0$$

$$+ Q_2 \cdot Q_1$$

$$+ Q_1 \cdot Q_0'$$

$$K_1 = J_1'$$

$Q_3 Q_2 Q_1 Q_0$	01	11	10	
000	0	0	1	0
001	0	0	0	0
010	0	0	0	0
011	0	0	0	0
100	1	0	0	0

$$J_2 = Q_3 \cdot Q_2' \cdot Q_1' \cdot Q_0' + Q_3' \cdot Q_2' \cdot Q_1 \cdot Q_0$$

$$K_2 = J_2'$$

$Q_3 Q_2 Q_1 Q_0$	01	11	10	
000	1	g	1	1
001	0	0	0	0
010	0	0	0	0
011	0	0	0	0
100	1	0	0	0

$$J_0 = g' \cdot Q_3' \cdot Q_2' \cdot Q_1' \cdot Q_0 + Q_2' \cdot Q_1' \cdot Q_0'$$

$$+ Q_3' \cdot Q_2' \cdot Q_1$$

$$K_0 = J_0'$$